

Capacitance



Capacitor:

A device/component that stores energy in the form of electric field.

Symbol



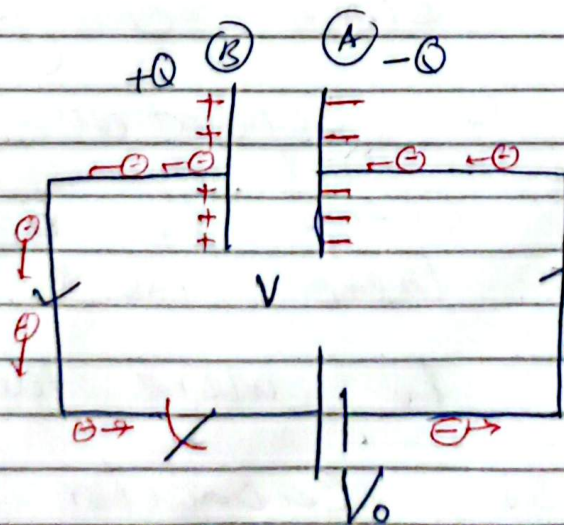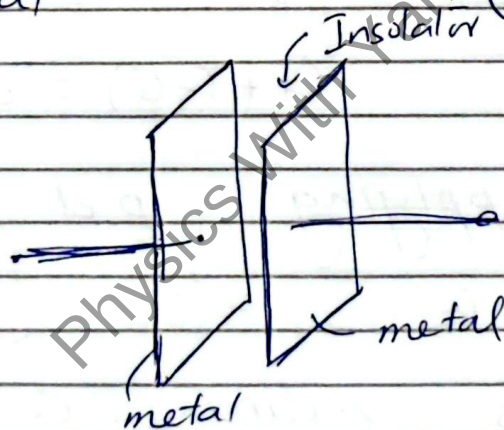It is made up of two metal plates which are held parallel and they are separated by insulating material.



When switch is closed

electrons flow towards plate A. It becomes $\ominus$ charge

when switch is closed:

Electrons move away from plate B so it becomes $\oplus$ charge

Flow of electrons will stop when potential difference between plates becomes equal to emf of battery.


total charge on both plates =

$$Q + (-Q) = 0$$

Before applying p.d total charge was also zero

so this means capacitor does not store charge

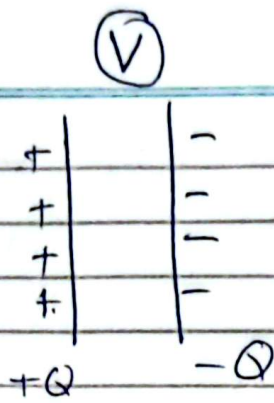But there is separation of $\oplus$ and $\ominus$ charge so this means there work has been done to move them apart so capacitor stores energy.



Due to charge on both plates
there is a potential difference
between them

$$Q \propto V$$

$$Q = CV$$

Where C is known as
capacitance

Capacitance

$$C = \frac{Q}{V}$$

Ratio of charge to potential
difference across capacitor.

unit is Farad (F)

Define Farad (F)


$$F = \frac{\text{Coulomb}}{\text{Volt}}$$

$$\boxed{C/V}$$


Micro farad $\rightarrow \mu F \rightarrow 10^{-6} F$

Nano farad $\rightarrow nF \rightarrow 10^{-9} F$

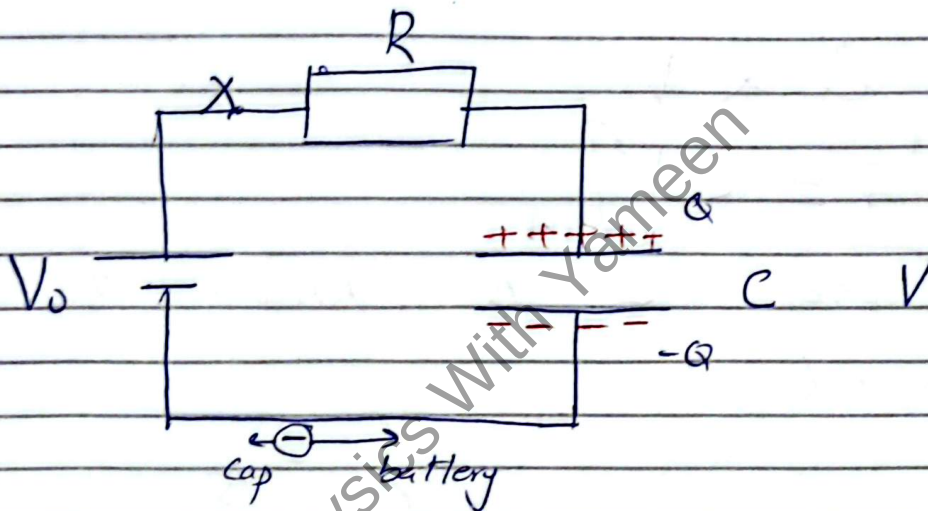
If we apply resistor in series to the circuit capacitor charging time will be controlled



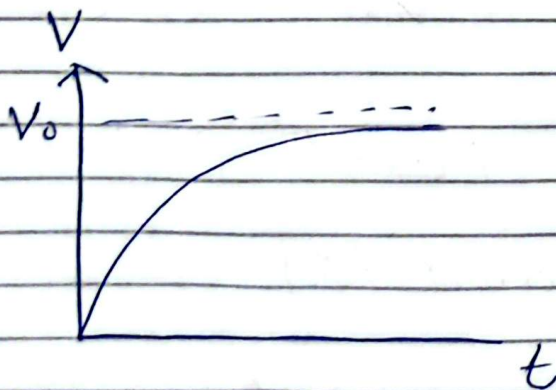
Voltage across capacitor will increase with time



V: Voltage across the capacitor

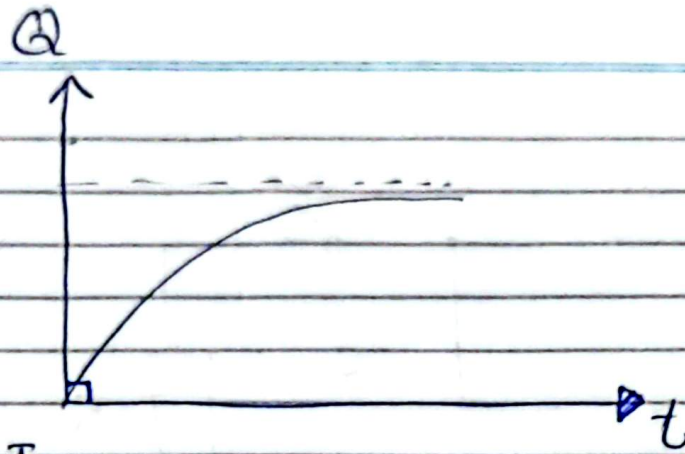


Rate of
Charge will
decrease with
time.

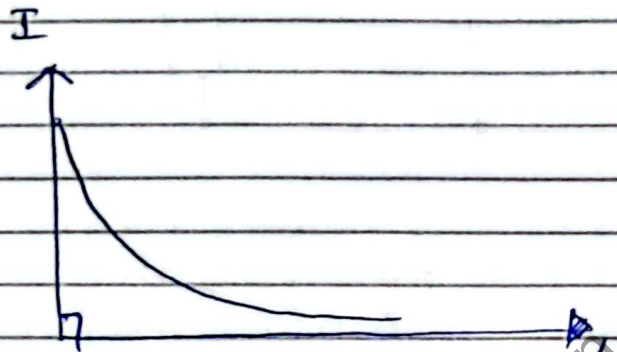

Physics With Yameer

Discharging of a capacitor

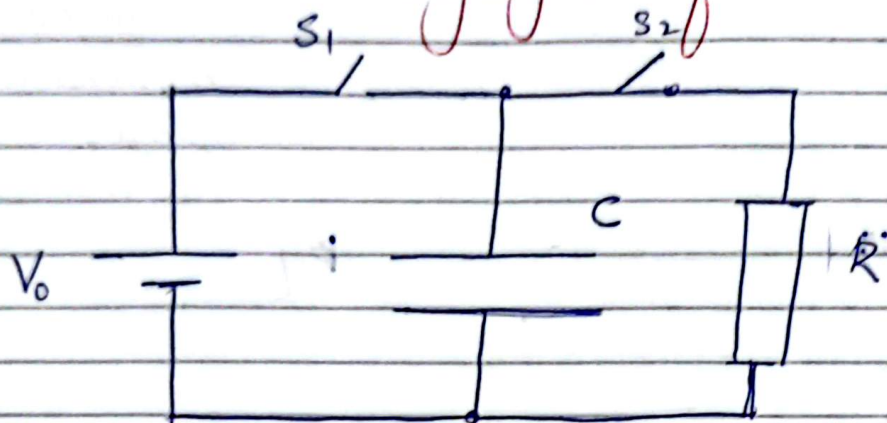


When S_1 is closed and S_2 is open the capacitor will charge upto V_0 .

When S_1 is opened and S_2 is closed the capacitor will discharge through R .

The voltage across the capacitor will decrease as charge decreases.

$$V = V_0 e^{-\frac{t}{RC}}$$

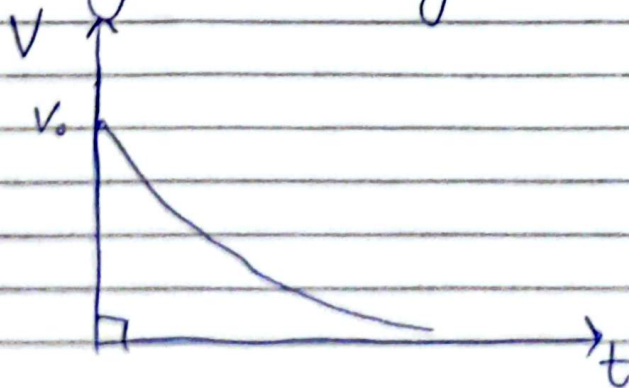This is voltage across capacitor during discharge at time t .



Rate of decrease of voltage is decreasing.

Time constant


product of R and C

$$\therefore \tau = RC$$

unit: second


Equation of charge

$$Q = Q_0 e^{-\frac{t}{RC}}$$

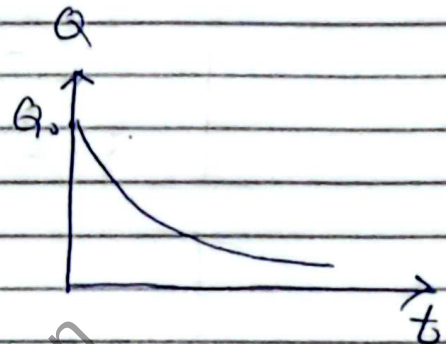

Current

$$I = I_0 e^{-\frac{t}{RC}}$$

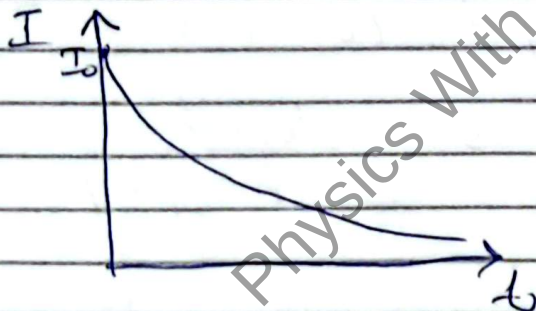


$$V = V_0 e^{-t/RC}$$

after one time constant $t = RC$

$$V = V_0 e^{-1}$$


$$V = 0.37 V_0$$

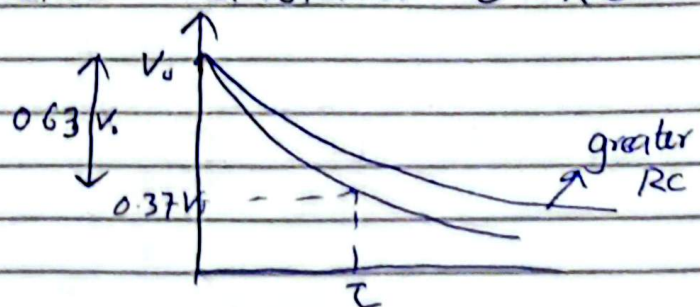

In one time constant capacitor

discharges by 63%

Example

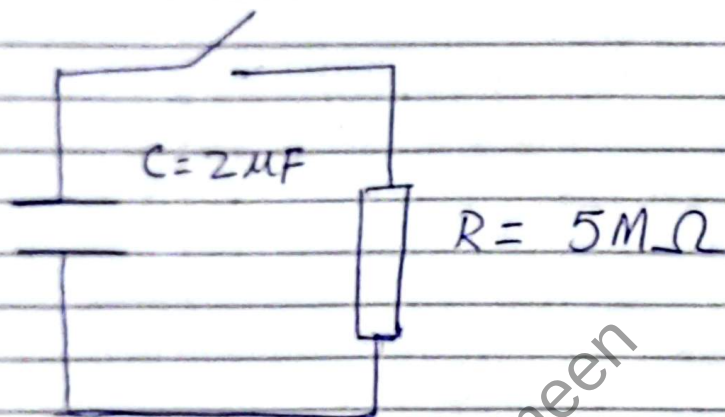

Capacitor is charged to 10 V

When switch is closed capacitor starts discharging

$$V = V_0 e^{-\frac{t}{RC}}$$

$$V_0 = 10V$$

$$V = 10 e^{-\frac{t}{5 \times 10^6 \times 2 \times 10^{-6}}}$$

Convert
R into Ω
C " F

$$V = 10 e^{-\frac{t}{10}}$$

Find voltage at these times

t	V
0	10
1	9.0
2	8.2
3	7.4
⋮	
10	3.7
⋮	
50	0.1

$$V = 10 e^{-\frac{t}{10}}$$

$$V = 10 e^{-\frac{1}{10}}$$

Find time at which voltage across the capacitor is 6V

$$V = V_0 e^{-t/RC}$$

$$V = 10 e^{-\frac{t}{10}}$$

$$6 = 10 e^{-\frac{t}{10}}$$

$$6 = 10 e^{-\frac{t}{10}}$$

$$\frac{6}{10} = e^{-\frac{t}{10}}$$

take $\ln$ on both sides


$$\ln\left(\frac{6}{10}\right) = \ln\left(e^{-\frac{t}{10}}\right)$$

$$\ln\left(\frac{6}{10}\right) = -\frac{t}{10} \ln e$$

$$t = 5.1 \text{ s}$$

Finding time constant from
graph : same for $(V-t)$ graph

$(\phi-t)$ "
 $(I-t)$ "

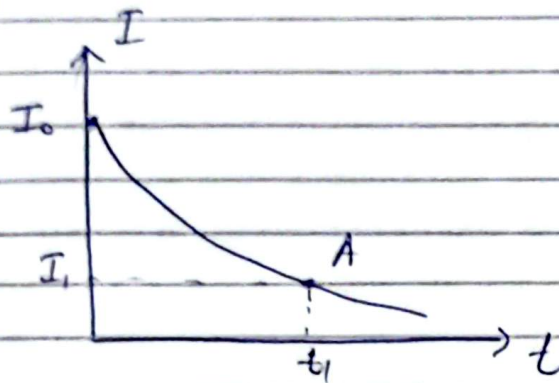

$$I = I_0 e^{-\frac{t}{\tau}}$$

$$RC = \tau$$

take any point
from the graph

lets take (A)

$$I_1 = I_0 e^{-\frac{t_1}{\tau}} \rightarrow (1)$$

$$I_0 = \text{known}$$

$$I_1 = "$$

$$t_1 = "$$

Unknown τ


solve eq (1) to get τ

$$V = V_0 e^{-\frac{t}{RC}}$$


$$\frac{V}{V_0} = e^{-\frac{t}{RC}}$$

$$\ln\left(\frac{V}{V_0}\right) = \ln\left(e^{-\frac{t}{RC}}\right)$$

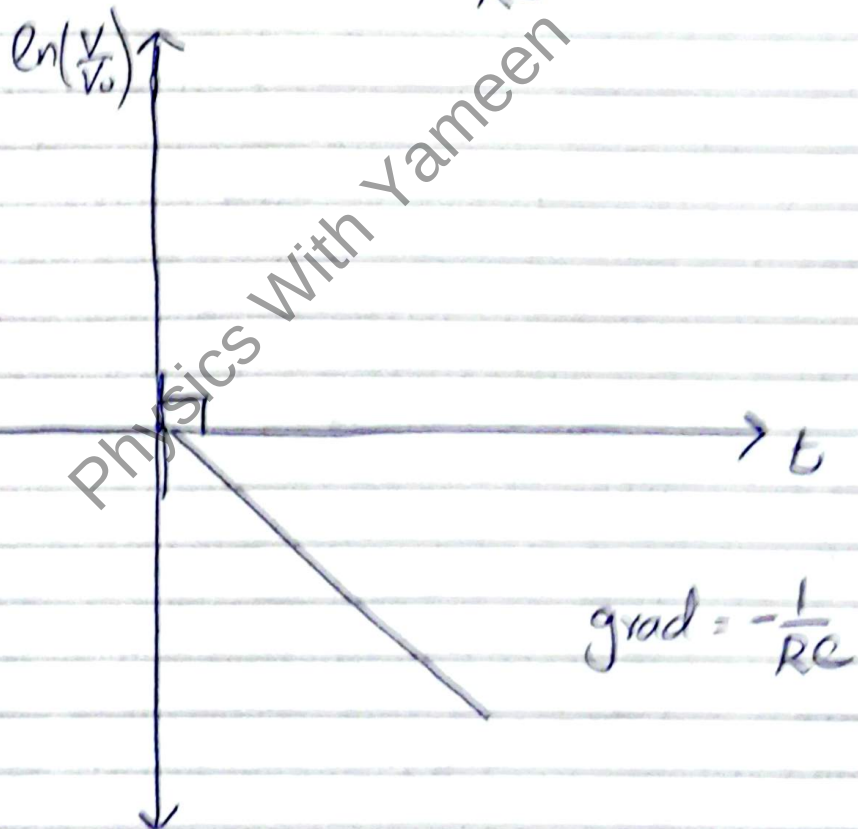
$$\ln\left(\frac{V}{V_0}\right) = -\frac{t}{RC} \ln e$$



$$y = -x$$

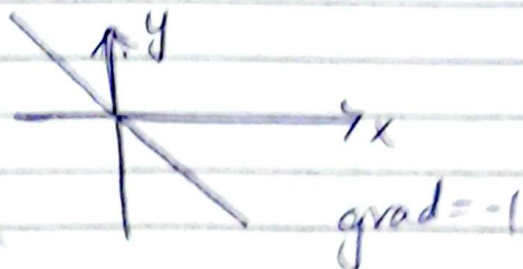

$$y = -2x$$

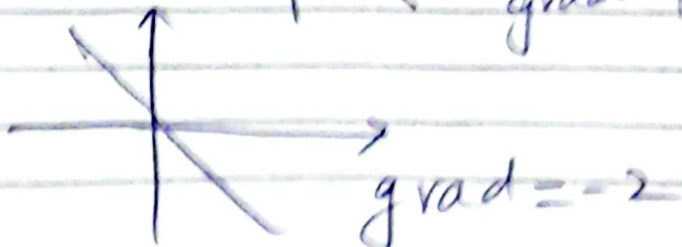


Combinations of capacitors

① Series

② parallel

Series

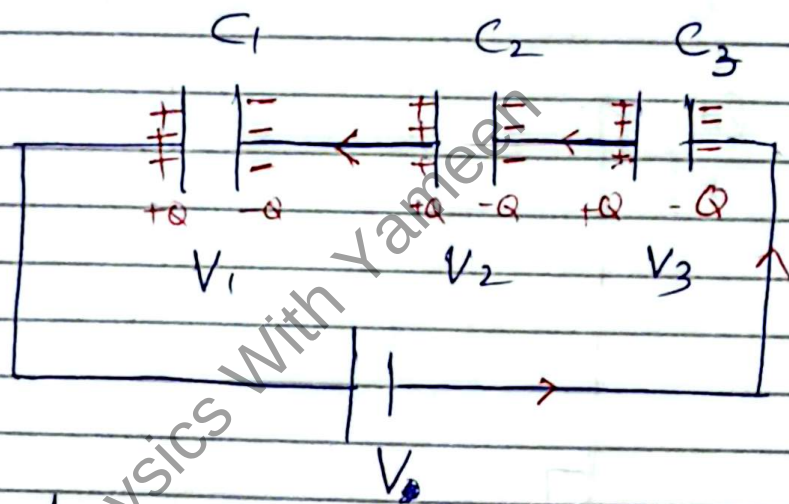

properties

- * charge across each capacitor is same
- * Voltage across each is different ($Q = CV$)

$$V = \frac{Q}{C}$$

Q is same

$$V \propto \frac{1}{C}$$

as capacitors are different
so V is different

$$V = V_1 + V_2 + V_3$$

$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$


$$\frac{V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\boxed{\frac{1}{C_{tot}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

For two capacitors in
Series

$$C_{tot} = \frac{C_1 C_2}{C_1 + C_2}$$


Product
Sum

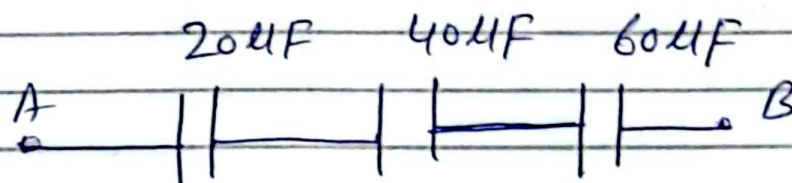

$$\frac{1}{C_{tot}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_{tot}} = \frac{1}{20} + \frac{1}{40} + \frac{1}{60}$$

$$C_{tot} = 10.9 \text{ uF}$$

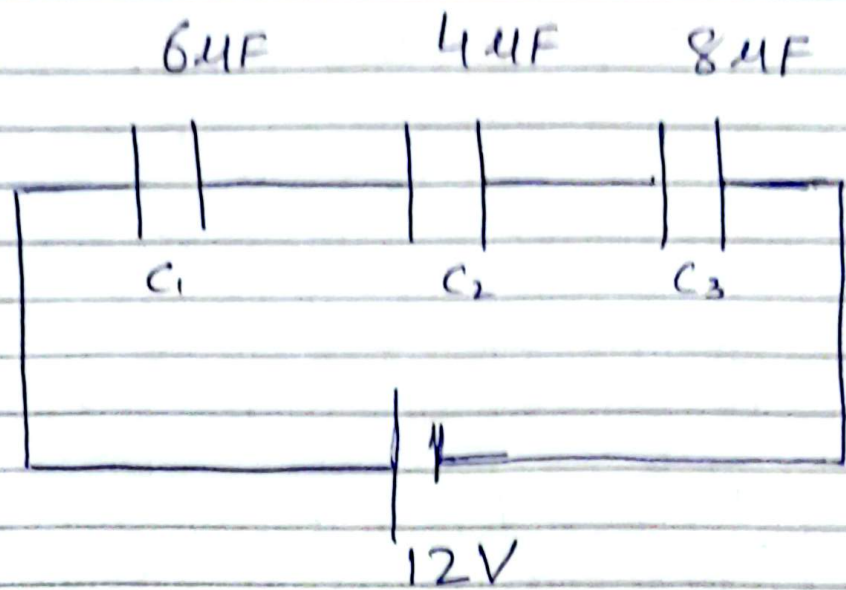

- i) Find total capacitance
- ii) Find total charge transferred by the battery
- iii) Find charge across each capacitor
- iv) Find potential difference across potential difference.

$$\frac{1}{C_{\text{tot}}} = \frac{1}{6} + \frac{1}{4} + \frac{1}{8}$$

$$C_{\text{tot}} = 1.85 \mu F \quad \text{or} \quad 1.85 \times 10^{-6} F$$

$$Q_{\text{tot}} = C_{\text{tot}} V$$

$$Q_{\text{tot}} = 1.85 \times 12 = 22.2 \mu C$$

Charge across each cap is
same as total charge.

$$Q = 22.2 \mu\text{C}$$

voltage across each

$$V_1 = \frac{Q}{C} = \frac{22.2 \mu\text{C}}{6 \mu\text{F}}$$


$$V_1 = \frac{22.2 \times 10^{-6} \text{ C}}{6 \times 10^{-6} \text{ F}}$$

$$V_1 = 3.7 \text{ V}$$

$$V_2 = \frac{Q}{C_2} = \frac{22.2}{4}$$

$$V_3 = \frac{Q}{C_3} = \frac{22.2}{8}$$

Capacitors in parallel.

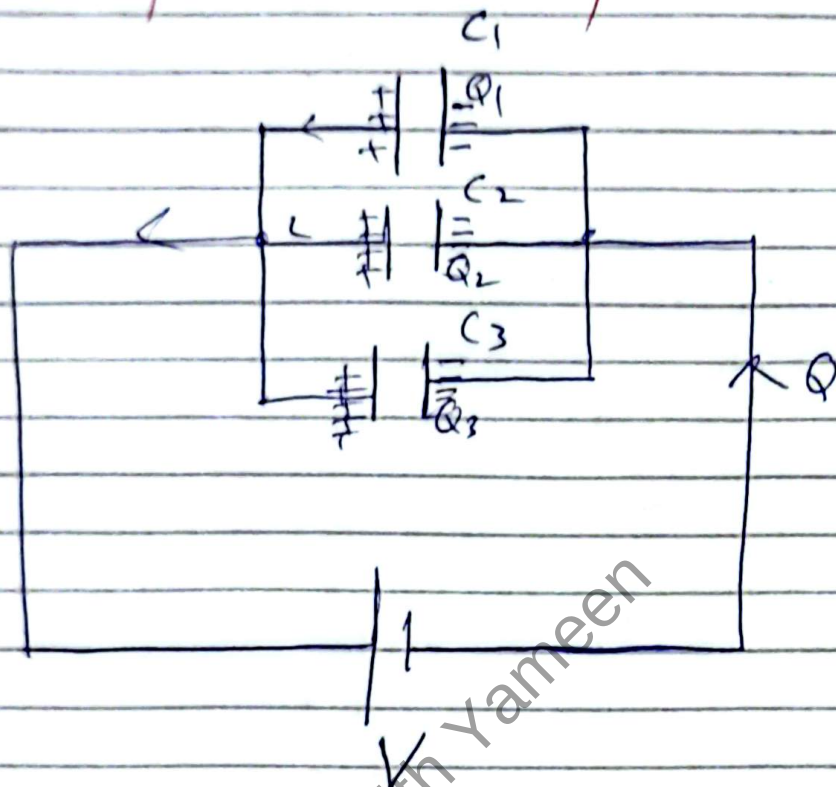

Properties

* p.d across each is same (V)

* $Q = CV$ Charge across each is different as V is same but C is different

$$Q \propto C$$


$$Q = Q_1 + Q_2 + Q_3$$

$$Q = C_1 V + C_2 V + C_3 V$$


$$\frac{Q}{V} = C_1 + C_2 + C_3$$

$$C_{\text{tot}} = C_1 + C_2 + C_3$$

Charge dividing

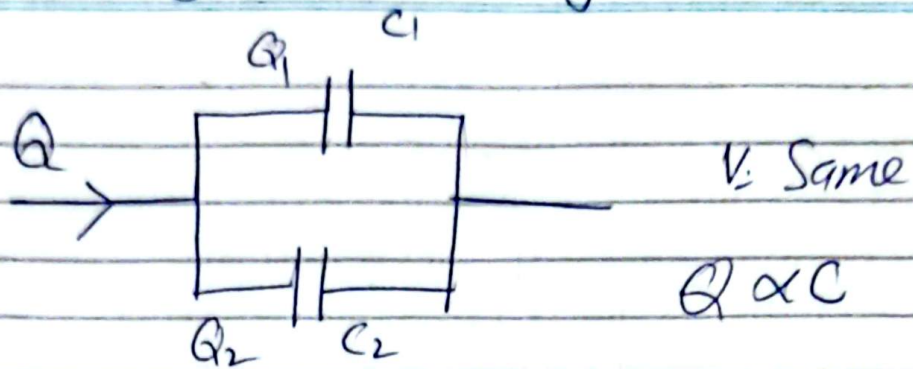
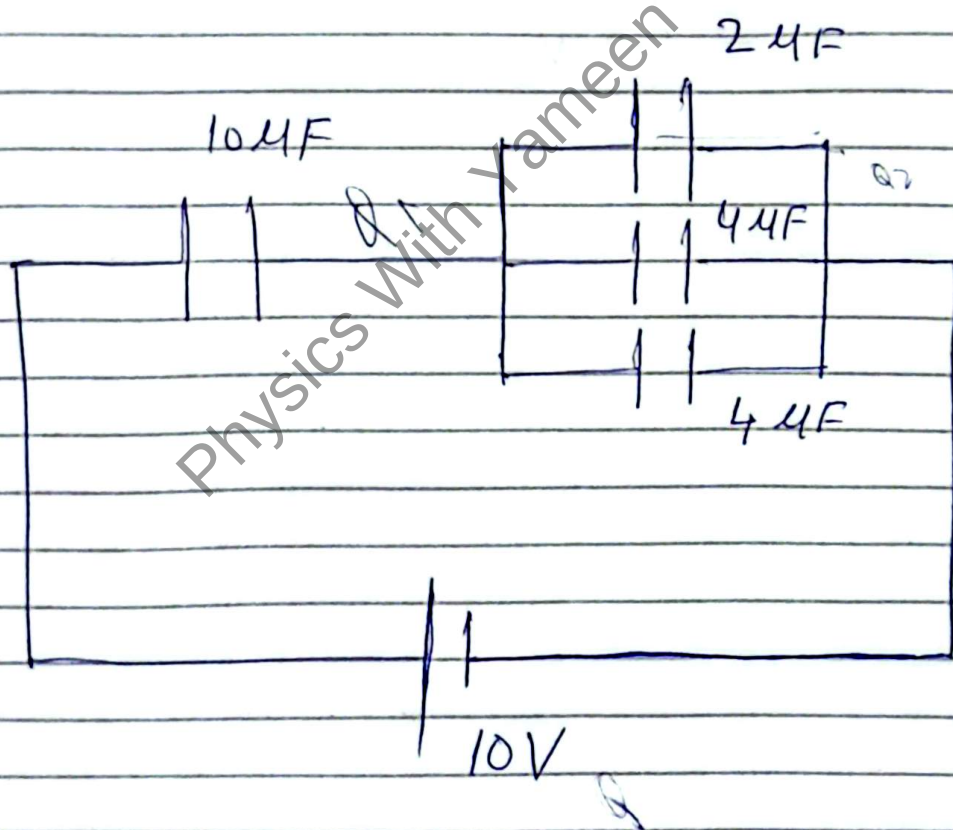
$$Q_1 = \frac{C_1}{C_1 + C_2} \times Q \quad Q = \text{total}$$




Find

- i) total capacitance
- ii) total charge
- iii) charge across each cap

iv) Voltage across each capacitor

2, 4, 4, are in parallel

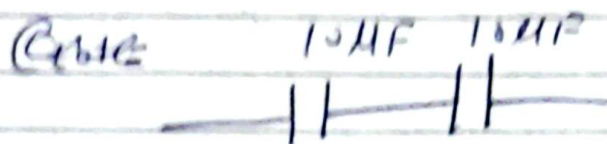

$$\frac{1}{C_{tot}} = \frac{1}{10} + \frac{1}{10}$$

$$\frac{1}{C_{tot}} = \frac{2}{10}$$

$$C_{tot} = 5\mu F$$

$$Q = C_{tot} \times V$$

$$= 5 \times 10$$

$$Q = 50\mu C$$

cap $10\mu F$ will have $50\mu C$ charge
but charge across 2, 4, 4 will distribute

$$V_{10\mu F} = \frac{Q}{C}$$

$$= \frac{50\mu C}{10\mu F} = 5V$$


$$Q_{2\mu F} = 5 \times 2 = 10\mu C$$

$$Q_{4\mu F} = 4 \times 5 = 20\mu C$$

$$Q_{4\mu F} = 4 \times 5 = 20\mu C$$

Charged Spherical conductors as capacitor.

Example: positively charged

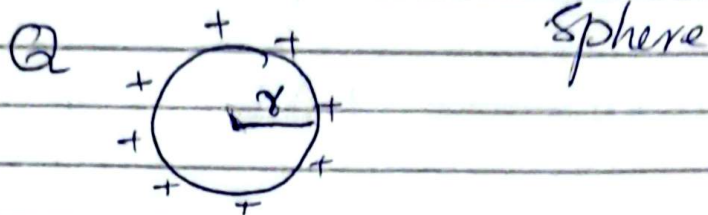

We assume the charge Q
is at the center

Electric potential at
surface ?

$$V = \frac{1}{4\pi\epsilon_0} \frac{Q}{r} \rightarrow$$


$$Q = CV$$

$$\frac{Q}{V} = C$$

$$4\pi\epsilon_0 r = \frac{Q}{V}$$

$$\boxed{4\pi\epsilon_0 r = C}$$


Energy stored in a capacitor.

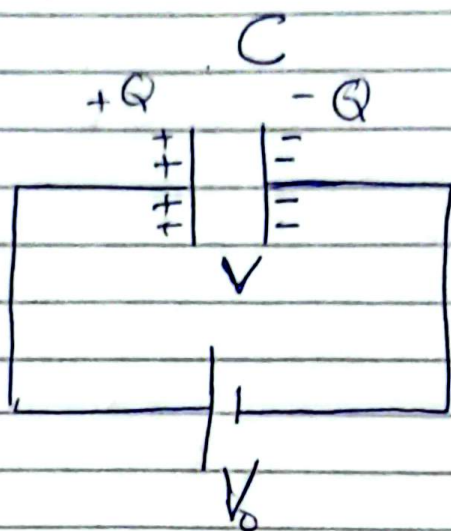

Charge on each plate is equal in magnitude but opposite in sign


battery does work to separate $\oplus$ and $\ominus$ charges
 this work done is stored in the form of Electric potential energy

$$Q = CV$$

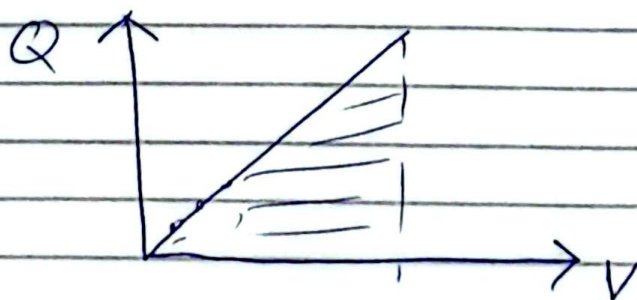

$$V = \frac{W}{Q}$$

$$W = VQ$$

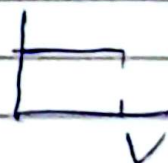

Area is equal to work done = $\frac{1}{2} QV$


$$\text{Energy stored} = \frac{1}{2} QV \rightarrow (1)$$

We know $Q = CV$

put in (1)

$$\text{Energy} = \frac{1}{2} CV \cdot V$$
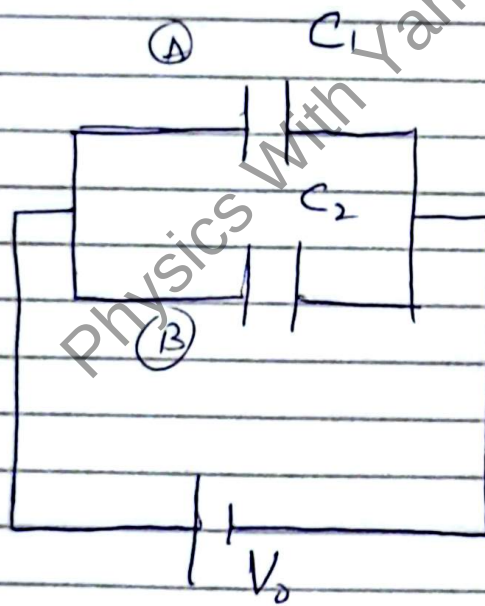
$$\boxed{\text{Energy} = \frac{1}{2} CV^2}$$




$E \propto C$
in this case
as V is same

$$\text{Energy stored in A} : \frac{1}{2} C_1 V_0^2$$

$$\text{" " " B} : \frac{1}{2} C_2 V_0^2$$
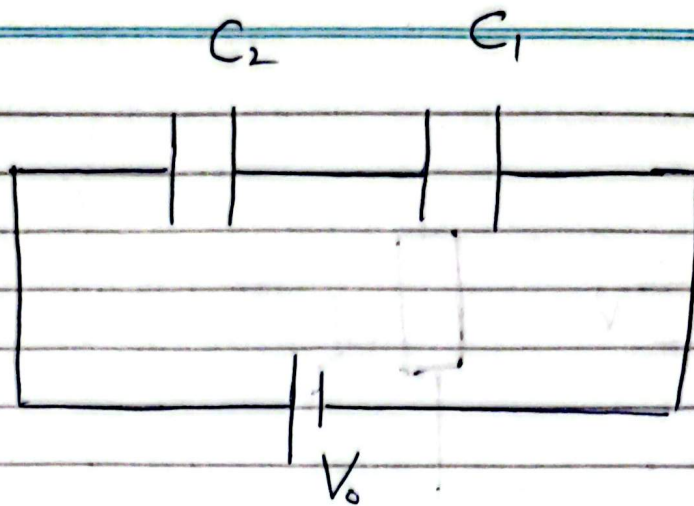
$$\text{Ratio} \quad \boxed{\frac{E_A}{E_B} = \frac{C_1}{C_2}}$$



In series charge is same.

but voltage is different


$$V \propto \frac{1}{C}$$

$$E = \frac{1}{2} QV$$

Q : same


$$E \propto \frac{V}{C}$$

$\frac{E_{C1}}{E_{C2}}$	$=$	$\frac{C_2}{C_1}$
-------------------------	-----	-------------------

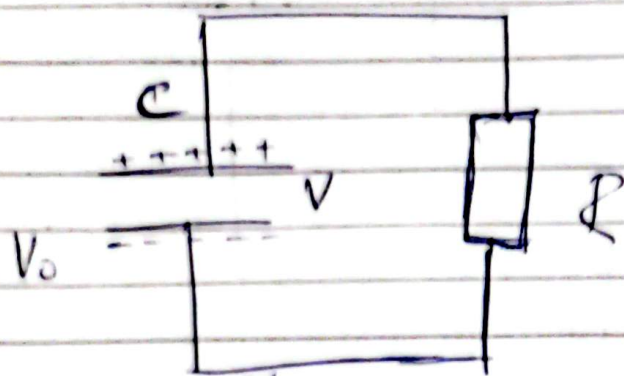

C: discharging

V₀: initial V₀

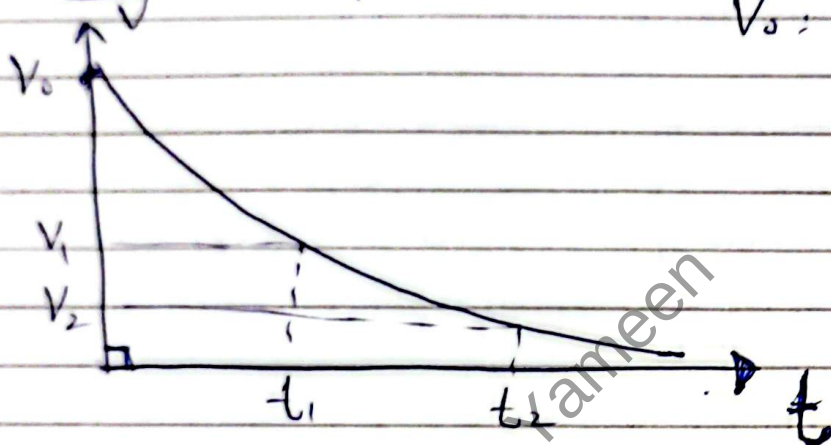


Find Loss of energy from
t₁ to t₂ ?

$$\text{at } t_1 : E_1 = \frac{1}{2} C V_1^2$$

$$\text{at } t_2 \quad E_2 = \frac{1}{2} C V_2^2$$

$$\text{Loss of energy} = \frac{1}{2} C V_1^2 - \frac{1}{2} C V_2^2$$

$$= \frac{1}{2} C (V_1^2 - V_2^2)$$

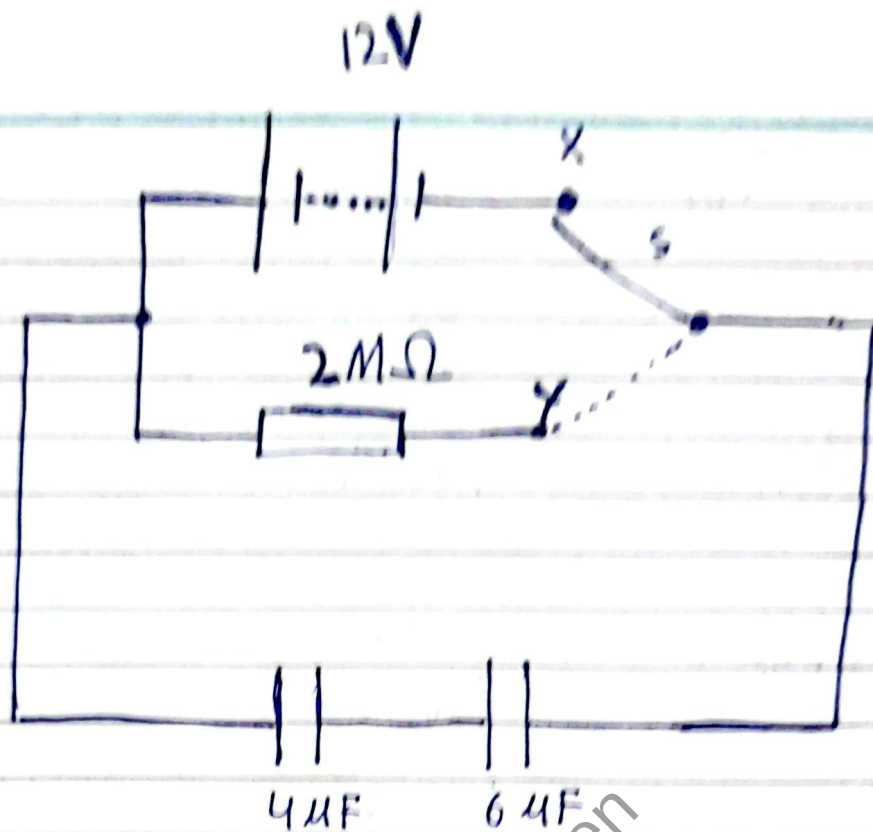

when switch is at x
both capacitor will charge

i) find voltage across each capacitor.

$$C_{tot} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$

$$\frac{1}{C_{tot}} = \frac{1}{4} + \frac{1}{6}$$

$$\frac{1}{C_{tot}} = \frac{3}{12} + \frac{2}{12}$$

$$C_{tot} = \frac{12}{5} = 2.4 \mu F$$

$$Q_{tot} = C_{tot} \times 12 = 2.4 \times 12 = 28.8 \mu C$$

$$V_{4F} = \frac{Q}{C}$$

$$= \frac{28.8}{4}$$

$$V_{4F} = 7.2 \text{ V}$$

$$V_{6\mu F} = \frac{28.8}{6}$$

$$V_{6\mu F} = 4.8 \text{ V}$$

When switch is connected is at y then capacitors will discharge.

Voltage across both cap will decrease

$$V = V_0 e^{-\frac{t}{RC_{tot}}}$$

$$V = 12 e^{-\frac{t}{2 \times 10^{-6} \times 2.4 \times 10^{-6}}}$$

$$V_{tot} = 12 \cdot e^{-\frac{t}{4.8}}$$

find total voltage at

$$t = 1s, \quad t = 10s, \quad t = 15s$$

$$V = 12 e^{-\frac{1}{4.8}}$$

$$V = 12 e^{-\frac{10}{4.8}}$$

$$V = 9.74V$$

$$V = 1.49V$$

at $t = 15s$

$$V = 12 e^{-\frac{15}{4.8}}$$

$$V = 0.527V$$

If we have to find
voltage across any capacitor

find voltage across 4μF at

$$t = 2s$$



There are two methods

- ① Find total voltage after 2s

$$V = V_0 e^{-t/R_{\text{tot}} C_{\text{tot}}}$$

$$V = 12 e^{-\frac{2}{4.8}}$$

$$V = 7.9 \text{ V}$$

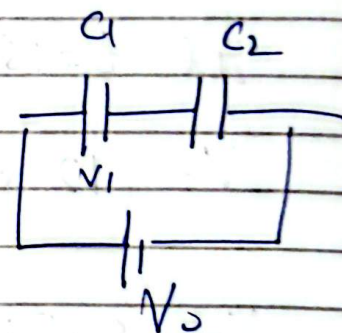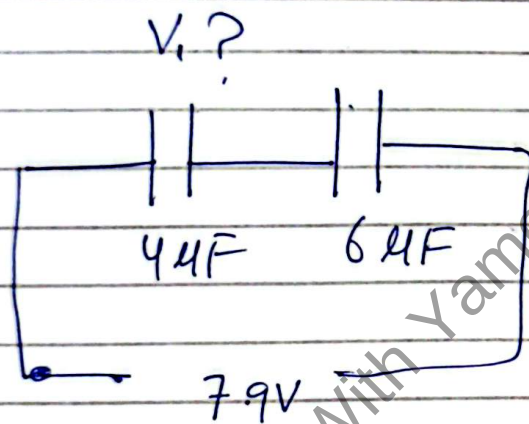

$$V_1 = \frac{6}{6+4} \times 7.9$$

$$V_1 = \frac{C_2}{C_1+C_2} \times V_0$$

$$V_1 = 4.74 \text{ V}$$

2nd Method

find initial voltage across

4 μF :

$$V_{4\mu\text{F}} = 7.2 \text{ V}$$

Use This


$$V_{u4F} = V_{04F} e^{-\frac{t}{RC_{tot}}}$$

$$V_{u4F} = 7.2 e^{-\frac{2}{4.8}}$$

$$V_{u4F} = 4.74$$

Same as
we got by
2nd method

Physics With Yameen

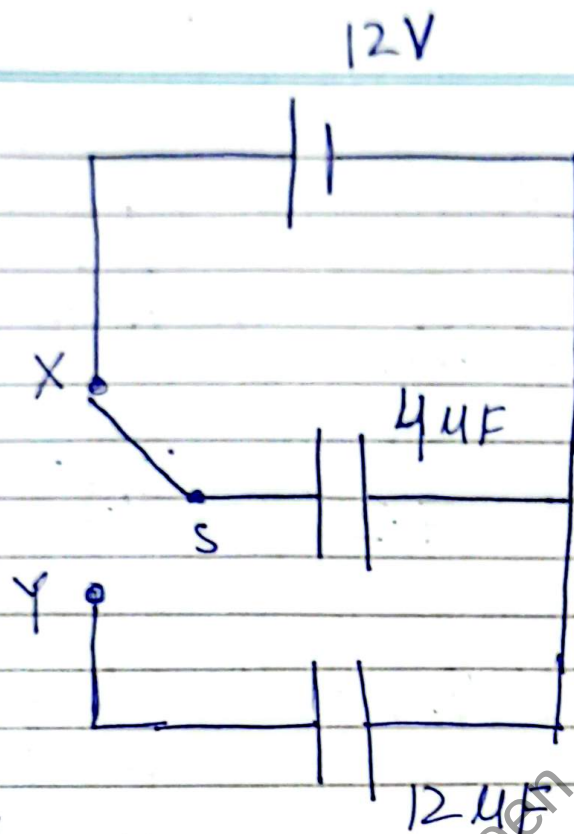

When switch is at X

$4 \mu F$ will get charge

$$Q = CV$$

$$Q = 4 \times 12 = 48 \mu C$$

When switch is connected at

Y $4 \mu F$ will discharge

and $12 \mu F$ will charge

This process will stop when
Potential difference

Final Charge across each will be different.
across both will be same.

If we have to find the final potential difference?

$$Q = Q_{4\mu F} + Q_{12\mu F}$$

$$Q = C_{4\mu F} V + C_{12\mu F} V$$

$$48 \mu F = 4 \mu F V + 12 \mu F V$$

$$48 \mu F = 16 \mu F V$$

$$48 \times 10^{-6} = 16 \times 10^{-6} V$$

$$\boxed{3 V = V}$$